

Project: pipelined RISC-V

1. Introduction

in the area of Computer Architecture, it was originally designed to support research and education, for academic and industrial applications RISC-V instruction set architecture (ISA) is now set to become a standard free and open architecture. For the success and adoption of RISC-V, 32-bit, 64-bit and 128-bit address spaces support by RISC-V.

A minimal set of instructions adequate to provide a reasonable target for assemblers, linkers, compilers and operating systems, the ISA is separated into a small base integer ISA. The set of compatible tool chains which includes the above Suits, provided by RISC-V foundation.

In this architecture it provides the following set of **RV32I instructions**:

R-Type: add, sub, and, or

I-Type: addi, andi, ori, lw, jalr

B-Type: beq, bne

J-Type: jal

S-Type: sw

You can add more instructions by modifying the architecture in terms of muxes and the width of control lines.


Pipeline RISC-V is an update of the single cycle RISC-V in terms of execution time and it's very fast for the programs that doesn't require forwarding the result of an instruction or using branches and jumps.

The pipeline RISC-V contains 5 stages:

- 1- Fetch (F)
- 2- Decode (D)
- 3- Execute (E)
- 4- Memory (M)
- 5- Writeback (W)


Every stage takes one smaller cycle to do its work. In the fetch stage we fetch the new instruction from the instruction memory. In the decode stage the processor read the operands from the register file and decode the instruction for the control unit. In the execute stage the ALU evaluates the output based on the operands and the ALUctrl. In the Memory stage data get saved in the data memory. In the writeback stage data get saved in the register file.

the combinational blocks between every stage and another works as one unit so the data will propagate together until the last stage. we can notice that the register file will be used twice in one instruction first it will read the operands in the decode stage and then save the data in the register file. So the best way to handle this situation is that the register file reads the operands at the positive edge of the clk and data is written back to the register file at the negative edge of the clock.

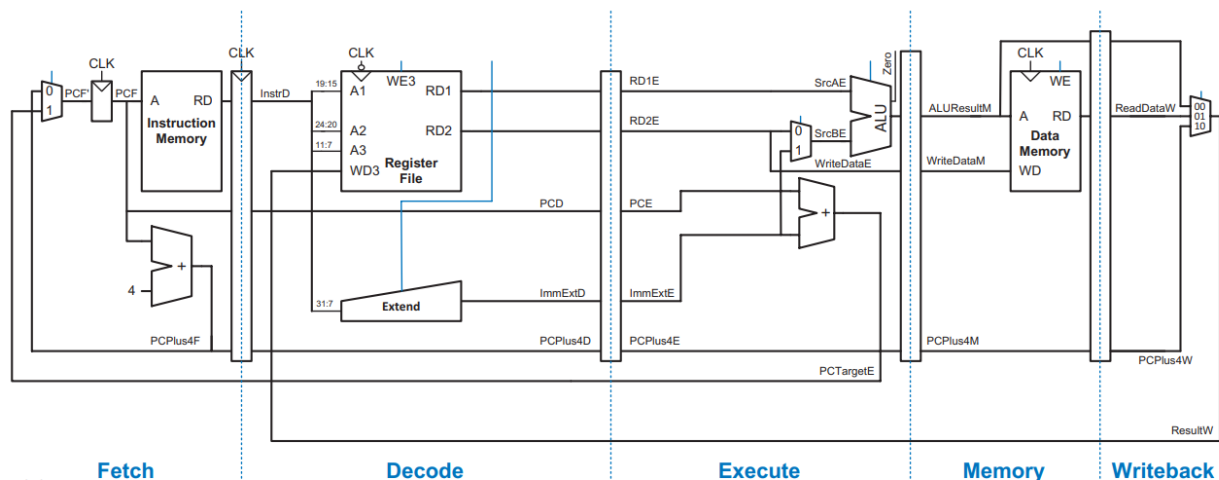


The pipeline architecture is different than the single cycle that it has **flip flops** between every stage and the next one so the data can propagate as one unit, and **two 3:1muxes** to select the operands for the ALU in case of the forwarding, and **hazard unit** to control the conditions of **forwarding, stalling, flushing**.

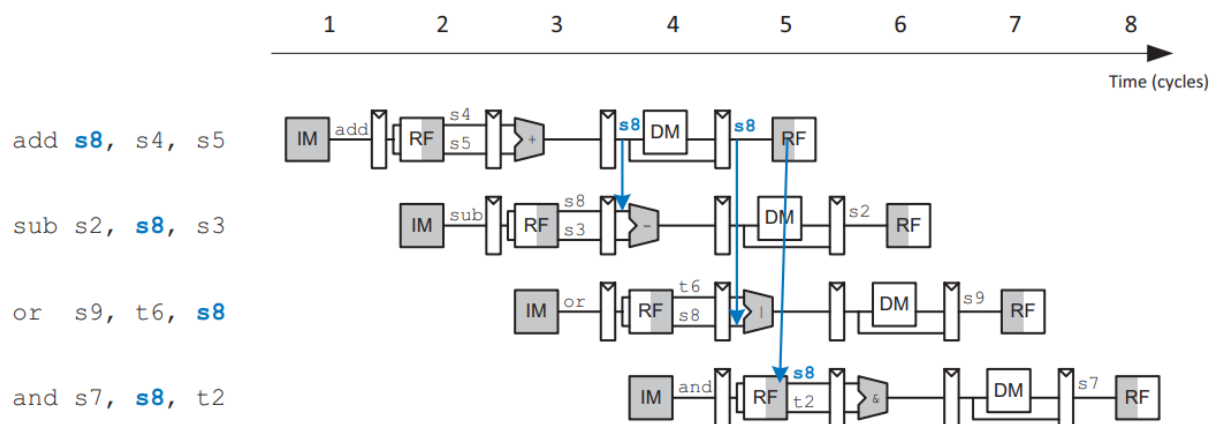
Forwarding is the case that the source register of an instruction in the execute stage(rs1E , rs2E) match the destination register of an instruction in the memory or writeback stage (rdM or rdW).



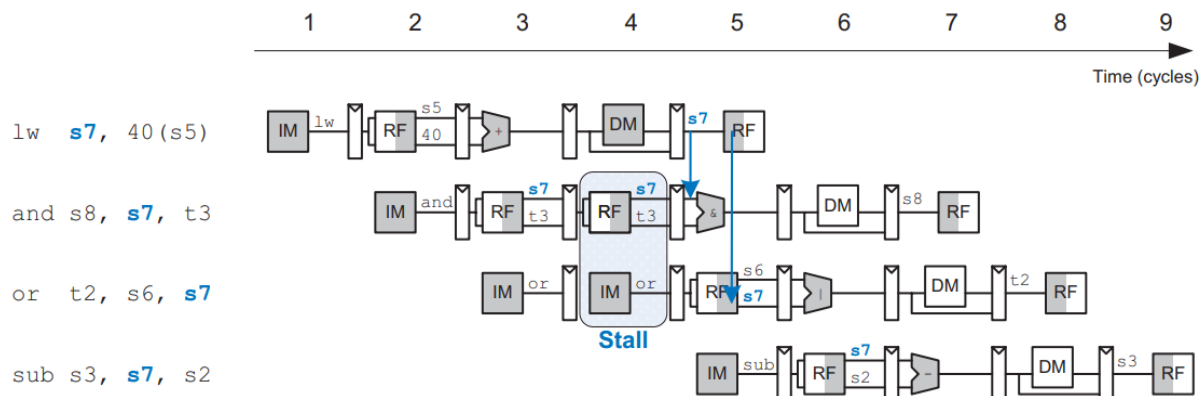Stalling is the case that we have to disable fetch and decode stage in order to give the load word instruction (lw) chance to read the data from the data memory as it can't be forward until the end of the memory stage. Flushing the execute stage by resetting its outputs will be necessary in this case to prevent the false data to interfere with the stalled data



Flushing is necessary in the case of branch instructions (beq) as the PC can't decide which instruction will be next whether it's the next instruction (PC+4) or the instruction at the new branch (PCtarget). So we should assume that the next instruction will be executed (PC+4) and continue as the branch will be false. In case of the branch is actually false then nothing will change, but in case the branch is true then we should flush the next two instructions and start fetching the new instruction in the branch and that will require to flush the decode and the execute stages.

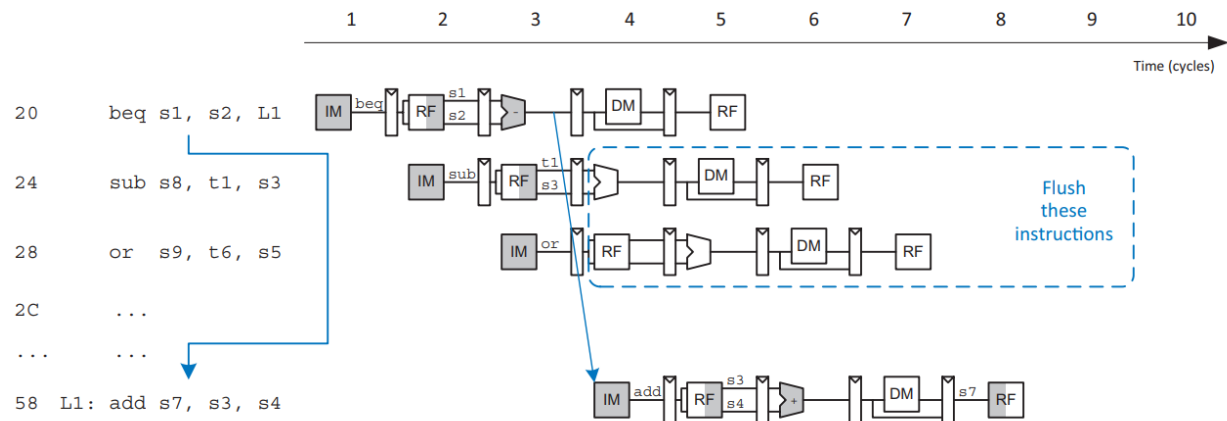

To calculate the execution time:

$$T_{exec} = \text{instructions} * CPI \left(\frac{\text{cycle}}{\text{instruction}} \right) * T_c \left(\frac{\text{seconds}}{\text{cycle}} \right)$$

In our example we testcase we have #instructions = 16 instructions , CPI = 1.25 (approximately for pipelined cycle), T_c is calculated by evaluate the critical path for the longest combinational logic between stages which is the excute stage.


$$T_c = t_{pcq_{pc}} + t_{alu} + 4t_{mux} + t_{and-or} + t_{setup}$$

$$T_c = 10 + 50 + 4 * 10 + 10 + 10 = 120 \text{ ps}$$

We can now evaluate the minimum execution time for our pipelined RISC-V:

$$T_{exec} = 16 * 1.25 * 120 = 2400 \text{ ps} = 2.4 \text{ ns}$$

2. Block diagram

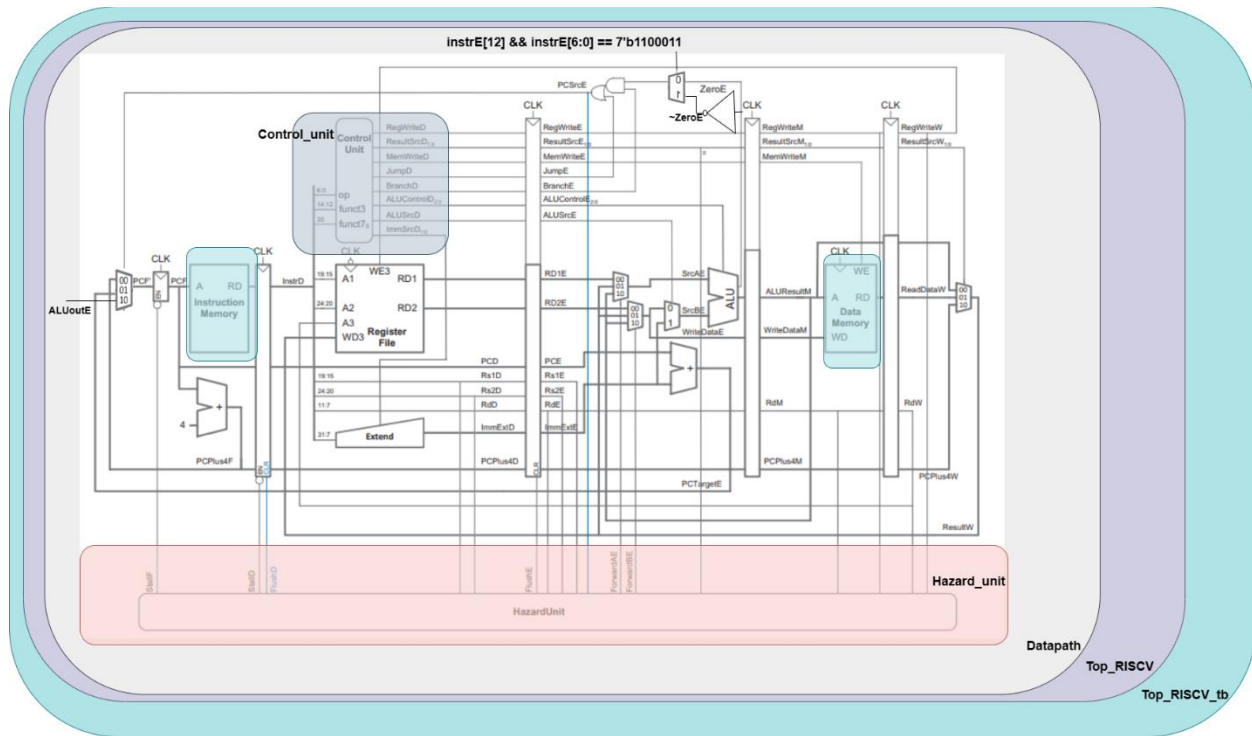

3. Design codes:

3.1 mux2x1

```

module mux2x1 #(parameter n = 32) (
input wire sel ,
input wire [n-1:0] in0 , in1 ,
output reg [n-1:0] out
);

always@(*)
begin
    if(sel)
        begin
            out = in1 ;
        end
    else
        begin
            out = in0 ;
        end
end

endmodule

```

3.2 mux3x1

```
module mux3x1 #(parameter n = 32) (  
  input wire [1:0] sel ,  
  input wire [n-1:0] in0 , in1 , in2,  
  output reg [n-1:0] out  
);  
  
always@(*)  
begin  
  if(sel == 2'b10 )  
    begin  
      out = in2 ;  
    end  
  else if (sel == 2'b01)  
    begin  
      out = in1 ;  
    end  
  else if (sel == 2'b00)  
    begin  
      out = in0 ;  
    end  
  else  
    begin  
      out = in0 ;  
    end  
end  
  
endmodule
```

3.3 flip flop

```
module flip_flop #(parameter n = 32) (  
  input wire clk,  
  input wire [n-1:0] d,  
  output reg [n-1:0] q  
);  
  
always@(posedge clk)  
begin  
  q <= d ;  
end  
  
endmodule
```

3.4 flip flop with reset

```
module flip_flop_rst #(parameter n = 32) (  
  input wire clk,  
  input wire rst,  
  input wire [n-1:0] d,  
  output reg [n-1:0] q  
);  
  
always@(posedge clk)  
begin  
  if(rst)  
    begin  
      q <= 0 ;  
    end  
  else  
    begin  
      q <= d ;  
    end  
end  
  
endmodule
```

3.5 flip flop with enable and reset

```
module flip_flop_en #(parameter n = 32) (  
  input wire clk,  
  input wire rst,  
  input wire en,  
  input wire [n-1:0] d,  
  output reg [n-1:0] q  
);  
  
always@(posedge clk or posedge rst)  
begin  
  if(rst)  
    begin  
      q <= 0 ;  
    end  
  else if(en)  
    begin  
      q <= d ;  
    end  
end  
  
endmodule
```

3.6 adder

```
module adder (  
  input wire [31:0] in1,  
  input wire [31:0] in2,  
  output wire [31:0] out  
);  
  
assign out = in1 + in2 ;  
  
endmodule
```

3.7 sign extend

```
module Sign_ext (  
  input wire [31:7] in,  
  input wire [1:0] opcode,  
  output reg [31:0] out  
);  
  
always@(*)  
begin  
  case(opcode)  
    2'b00 : //I-type instruction  
      out = { {20{in[31]}} , in[31:20] } ;  
    2'b01 : //S-type instruction  
      out = { {20{in[31]}} , in[31:25] , in[11:7] } ;  
    2'b10 : //B-type instruction  
      out = { {20{in[31]}} , in[7] , in[31:25] , in[11:8] , 1'b0 } ;  
    2'b11 : //J-type instruction  
      out = { {12{in[31]}} , in[19:12] , in[20] , in[30:21] , 1'b0 } ;  
    default : out = 32'hxxxxxxxx ;  
  endcase  
end  
  
endmodule
```

3.8 reg file

```
module Reg_file (
    input wire      clk,
    input wire [4:0] Addr1,
    input wire [4:0] Addr2,
    input wire [4:0] Addr3,
    input wire [31:0] wd3,
    input wire      we3,
    output reg [31:0] rd1,
    output reg [31:0] rd2
);

reg [31:0] temp [0:31] ;
integer i ;
//clocked writing
always@(negedge clk )
begin
    if(we3)
        begin
            temp[Addr3] <= wd3 ;
        end
end
//combinational reading
always@(*)
begin
    if(Addr1 == 0)
        begin
            rd1 = 0 ;
        end
    else
        begin
            rd1 = temp[Addr1] ;
        end

    if(Addr2 == 0)
        begin
            rd2 = 0 ;
        end
    else
        begin
            rd2 = temp[Addr2] ;
        end
end
endmodule
```

3.9 ALU

```
module Alu (
    input wire [1:0] ALUctrl ,
    input wire [31:0] A , B ,
    output reg [31:0] ALUout,
    output wire      zero
);
assign zero = (ALUout == 0)? 1 : 0 ;
always@(*)
begin
    case(ALUctrl)
        2'b00: ALUout = A + B ;
        2'b01: ALUout = A - B ;
        2'b10: ALUout = A & B ;
        2'b11: ALUout = A | B ;
        default: ALUout = 0 ;
    endcase
end
endmodule
```


3.10 main decoder

```
module main_decoder (
input wire [6:0] op,
output reg      jump,
output reg      jalr,
output reg      branch,
output reg [1:0] immsrc,
output reg      ALUsrc,
output reg [1:0] ALUop,
output reg [1:0] resultsrc,
output reg      regwr,
output reg      memwr
);

always@(*)
begin
case (op)
7'b0000011 : //lw instruction
begin
regwr      = 1'b1 ;
immsrc     = 2'b00 ;
ALUsrc     = 1'b1 ;
memwr      = 1'b0 ;
resultsrc  = 2'b01 ;
branch     = 1'b0 ;
ALUop      = 2'b00 ;
jump       = 1'b0 ;
jalr       = 1'b0 ;
end
7'b0100011 : //sw instruction
begin
regwr      = 1'b0 ;
immsrc     = 2'b01 ;
ALUsrc     = 1'b1 ;
memwr      = 1'b1 ;
resultsrc  = 2'bxx ;
branch     = 1'b0 ;
ALUop      = 2'b00 ;
jump       = 1'b0 ;
jalr       = 1'b0 ;
end
7'b0110011 : //R-type instruction
begin
regwr      = 1'b1 ;
immsrc     = 2'bxx ;
ALUsrc     = 1'b0 ;
memwr      = 1'b0 ;
resultsrc  = 2'b00 ;
branch     = 1'b0 ;
ALUop      = 2'b10 ;
jump       = 1'b0 ;
jalr       = 1'b0 ;
end
7'b1100011 : //beq instruction
begin
regwr      = 1'b0 ;
immsrc     = 2'b10 ;
ALUsrc     = 1'b0 ;
memwr      = 1'b0 ;
resultsrc  = 2'bxx ;
branch     = 1'b1 ;
ALUop      = 2'b01 ;
jump       = 1'b0 ;
jalr       = 1'b0 ;
end
end
```

```

    7'b0010011 : //I-type instruction (except jalr)
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b00 ;
    ALUsrc     = 1'b1 ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b00 ;
    branch     = 1'b0 ;
    ALUop      = 2'b10 ;
    jump       = 1'b0 ;
    jalr       = 1'b0 ;
end
7'b1101111 : //jal instruction
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b11 ;
    ALUsrc     = 1'bx ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b10 ;
    branch     = 1'b0 ;
    ALUop      = 2'bxx ;
    jump       = 1'b1 ;
    jalr       = 1'b0 ;
end
7'b1100111 : //jalr instruction
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b00 ;
    ALUsrc     = 1'b1 ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b10 ;
    branch     = 1'b0 ;
    ALUop      = 2'b00 ;
    jump       = 1'b0 ;
    jalr       = 1'b1 ;
end

default :
begin
    regwr      = 1'bx ;
    immsrc     = 2'bx ;
    ALUsrc     = 1'bx ;
    memwr      = 1'bx ;
    resultsrc  = 2'bx ;
    branch     = 1'bx ;
    ALUop      = 2'bx ;
    jump       = 1'bx ;
    jalr       = 1'bx ;
end
endcase
end

endmodule

```

3.11 ALU decoder

```

module Alu_decoder (
    input wire [1:0] ALUop,
    input wire [2:0] funct3,
    input wire      funct7_5,
    input wire      op_5,
    output reg [1:0] ALUctrl
);

always@(*)
begin
    case (ALUop)
        2'b00 : ALUctrl = 2'b00 ; //adding for lw,sw,jalr
        2'b01 : ALUctrl = 2'b01 ; //subtracting for beq,bne

```

```

2'b10 : //R,I-type instructions
begin
  case(func3)
    3'b000 :
      begin
        if({op_5,func7_5} == 3'b11)
          begin
            ALUctrl = 2'b01 ; //subtraction for sub
          end
        else
          begin
            ALUctrl = 2'b00 ; //adding for add,addi
          end
        end
      3'b111 : ALUctrl = 2'b10 ;//anding for and,andi
      3'b110 : ALUctrl = 2'b11 ;//oring for or,ori
      default : ALUctrl = 2'bxx ;
    endcase
  end
  default : ALUctrl = 2'bxx ;
endcase
end
endmodule

```

3.12 data_path

```

module datapath (
//global inputs
input wire clk,
input wire rst,
//instr memory inputs
input wire [31:0] instrF,
//data memory inputs
input wire [31:0] read_dataM,
//CU inputs
input wire [1:0] immsrcD,
input wire      ALUsrcD,
input wire [1:0] ALUctrlD,
input wire [1:0] resultsrcD,
input wire      regwrD,
input wire      jumpD,
input wire      jalrD,
input wire      branchD,
input wire      memwrD,
//hazard unit inputs
input wire [1:0] forwardAE,
input wire [1:0] forwardBE,
input wire      stallF,
input wire      stallD,
input wire      flushE,
input wire      flushD,
//CU outputs
output wire [31:0] instrD,
//hazard unit outputs
output wire [4:0] rs1E,
output wire [4:0] rs2E,
output wire [4:0] rdM,
output wire [4:0] rdW,
output wire      regwrM,
output wire      regwrW,
output wire [4:0] rs1D,
output wire [4:0] rs2D,
output wire [4:0] rdE,
output wire      resultsrcE0,
output wire      PCsrcE0,
//instr memory outputs
output wire [31:0] PCF,
//data memory outputs
output wire [31:0] ALUoutM,
output wire [31:0] write_dataM,
output wire      memwrM
);

```

```

wire [31:0] PCnext , PCplus4F , PCplus4D , PCplus4E , PCplus4M , PCplus4W, PCtargetE , PCD, PCE ;
wire [31:0] resultW ;
wire [31:0] SrcA , SrcB ;
wire [31:0] immextD , immextE ;

wire [31:0] instrE ;
wire jalrE ,branchE , jumpE,regwrE , memwrE , ALUsrcE ;
wire [31:0] rd1D, rd2D ,rd1E, rd2E ;
wire [31:0] ALUoutE , ALUoutW;
wire [31:0] write_dataE ;
wire [1:0] PCsrcE , ALUctrlE;
wire [1:0] resultsrcE , resultsrcM , resultsrcW ;
wire [31:0] read_dataW ;
wire [4:0] rdD ;

wire zero ;
wire zero_new ;
assign zero_new = (instrE[12] && instrE[6:0] == 7'b1100011)? !zero : zero ;
assign PCsrcE = {jalrE, ((zero_new & branchE) | jumpE) } ;

assign resultsrcE0 = resultsrcE[0] ;
assign PCsrcE0 = PCsrcE[0] ;
assign rs1D = instrD[19:15] ;
assign rs2D = instrD[24:20] ;
assign rdD = instrD[11:7] ;

//flip flops between fetch and decode
flip_flop_en #(32) u_ff1(
.clk(clk),
.rst(flushD),
.en(~stallD),
.d(instrF),
.q(instrD)
);

flip_flop_en #(32) u_ff2(
.clk(clk),
.rst(flushD),
.en(~stallD),
.d(PCF),
.q(PCD)
);

flip_flop_en #(32) u_ff3(
.clk(clk),
.rst(flushD),
.en(~stallD),
.d(PCplus4F),
.q(PCplus4D)
);

//flip flops between decode and excute
flip_flop_rst #(1) u_ff4(
.clk(clk),
.rst(flushE),
.d(regwrD),
.q(regwrE)
);

flip_flop_rst #(2) u_ff5(
.clk(clk),
.rst(flushE),
.d(resultsrcD),
.q(resultsrcE)
);

```

```

flip_flop_rst #(1) u_ff6(
.clk(clk),
.rst(flushE),
.d(memwrD),
.q(memwrE)
);

flip_flop_rst #(1) u_ff7(
.clk(clk),
.rst(flushE),
.d(jumpD),
.q(jumpE)
);

flip_flop_rst #(1) u_ff8(
.clk(clk),
.rst(flushE),
.d(jalrD),
.q(jalrE)
);

flip_flop_rst #(1) u_ff9(
.clk(clk),
.rst(flushE),
.d(branchD),
.q(branchE)
);

flip_flop_rst #(2) u_ff10(
.clk(clk),
.rst(flushE),
.d(ALUctrlD),
.q(ALUctrlE)
);

flip_flop_rst #(1) u_ff11(
.clk(clk),
.rst(flushE),
.d(ALUsrcD),
.q(ALUsrcE)
);

flip_flop_rst #(32) u_ff12(
.clk(clk),
.rst(flushE),
.d(rd1D),
.q(rd1E)
);

flip_flop_rst #(32) u_ff13(
.clk(clk),
.rst(flushE),
.d(rd2D),
.q(rd2E)
);

flip_flop_rst #(32) u_ff14(
.clk(clk),
.rst(flushE),
.d(PCD),
.q(PCE)
);

flip_flop_rst #(5) u_ff15(
.clk(clk),
.rst(flushE),
.d(rs1D),
.q(rs1E)
);

```

```

flip_flop_rst #(5) u_ff16(
.clk(clk),
.rst(flushE),
.d(rs2D),
.q(rs2E)
);

flip_flop_rst #(5) u_ff17(
.clk(clk),
.rst(flushE),
.d(rdD),
.q(rdE)
);

flip_flop_rst #(32) u_ff18(
.clk(clk),
.rst(flushE),
.d(immextD),
.q(immextE)
);

flip_flop_rst #(32) u_ff19(
.clk(clk),
.rst(flushE),
.d(instrD),
.q(instrE)
);

flip_flop_rst #(32) u_ff20(
.clk(clk),
.rst(flushE),
.d(PCplus4D),
.q(PCplus4E)
);
//flip flops between excute and memory
flip_flop #(1) u_ff21(
.clk(clk),
.d(regwrE),
.q(regwrM)
);

flip_flop #(2) u_ff22(
.clk(clk),
.d(resultsrcE),
.q(resultsrcM)
);

flip_flop #(1) u_ff23(
.clk(clk),
.d(memwrE),
.q(memwrM)
);

flip_flop #(32) u_ff24(
.clk(clk),
.d(ALUoutE),
.q(ALUoutM)
);

flip_flop #(32) u_ff25(
.clk(clk),
.d(write_dataE),
.q(write_dataM)
);

flip_flop #(5) u_ff26(
.clk(clk),
.d(rdE),
.q(rdM)
);

```

```

flip_flop #(32) u_ff27(
.clk(clk),
.d(PCplus4E),
.q(PCplus4M)
);

//flip flops between memory and writeback
flip_flop #(1) u_ff28(
.clk(clk),
.d(regwrM),
.q(regwrW)
);

flip_flop #(2) u_ff29(
.clk(clk),
.d(resultsrcM),
.q(resultsrcW)
);

flip_flop #(32) u_ff30(
.clk(clk),
.d(ALUoutM),
.q(ALUoutW)
);

flip_flop #(32) u_ff31(
.clk(clk),
.d(read_dataM),
.q(read_dataW)
);

flip_flop #(5) u_ff32(
.clk(clk),
.d(rdM),
.q(rdW)
);

flip_flop #(32) u_ff33(
.clk(clk),
.d(PCplus4M),
.q(PCplus4W)
);

flip_flop_en #(32) u_ff(
.clk(clk),
.rst(rst),
.en(~stallF),
.d(PCnext),
.q(PCF)
);

mux3x1 #(32) u_pcmux (
.sel(PCsrcE),
.in0(PCplus4F),
.in1(PCTargetE),
.in2({ALUoutE[31:1],1'b0}),
.out(PCnext)
);

Reg_file u_regf (
.clk(clk),
.Addr1(rs1D),
.Addr2(rs2D),
.Addr3(rdW),
.wd3(resultW),
.we3(regwrW),
.rd1(rd1D),
.rd2(rd2D)
);

```

```

Sign_ext u_signext(
.in(instrD[31:7]),
.opcode(immsrcD),
.out(immextD)
);

mux3x1 #(32) u_forwardAEmux (
.sel(forwardAE) ,
.in0(rd1E) ,
.in1(resultW) ,
.in2(ALUoutM) ,
.out(SrcA)
);

mux3x1 #(32) u_forwardBEmux (
.sel(forwardBE) ,
.in0(rd2E) ,
.in1(resultW) ,
.in2(ALUoutM) ,
.out(write_dataE)
);

mux2x1 #(32) u_alumux (
.sel(ALUsrcE) ,
.in0(write_dataE) ,
.in1(immextE) ,
.out(SrcB)
);

adder u_adderplus4 (
.in1(PCF),
.in2(32'd4),
.out(PCplus4F)
);

adder u_addertarget (
.in1(PCE),
.in2(immextE),
.out(PCtargetE)
);

Alu u_ALU (
.ALUctrl(ALUctrlE) ,
.A(SrcA) ,
.B(SrcB) ,
.ALUout(ALUoutE) ,
.zero(zero)
);

mux3x1 #(32) u_resultmux (
.sel(resultsrcW) ,
.in0(ALUoutW) ,
.in1(read_dataW) ,
.in2(PCplus4W) ,
.out(resultW)
);

endmodule

```


3.13 control_unit

```
module control_unit(
//instr memory inputs
input wire [6:0] opD,
input wire [2:0] funct3D,
input wire      funct7_5D,
//datapath outputs
output wire [1:0] immsrcD,
output wire      ALUsrcD,
output wire [1:0] ALUctrlD,
output wire [1:0] resultsrcD,
output wire      regwrD,
output wire      jumpD,
output wire      jalrD,
output wire      branchD,
//data memory output
output wire      memwrD
);

wire [1:0] ALUopD ;

main_decoder u_md (
.op(opD),
.jump(jumpD),
.jalr(jalrD),
.branch(branchD),
.immsrc(immsrcD),
.ALUsrc(ALUsrcD),
.ALUop(ALUopD), //
.resultsrc(resultsrcD),
.regwr(regwrD),
.memwr(memwrD)
);

Alu_decoder u_ad (
.ALUop(ALUopD),
.funct3(funct3D),
.funct7_5(funct7_5D),
.op_5(opD[5]),
.ALUctrl(ALUctrlD)
);

endmodule
```

3.14 hazard unit

```
module hazard_unit (
//fowarding inputs
input wire      rst,
input wire [4:0] rs1E,
input wire [4:0] rs2E,
input wire [4:0] rdM,
input wire [4:0] rdW,
input wire      regwrM,
input wire      regwrW,
//stalling inputs
input wire [4:0] rs1D,
input wire [4:0] rs2D,
input wire [4:0] rdE,
input wire      resultsrcE0,
//flushing inputs
input wire      PCsrcE0,
```

```

//forwarding outputs
output reg [1:0] forwardAE,
output reg [1:0] forwardBE,
//stalling outputs
output reg      stallF ,
output reg      stallD,
output reg      flushE,
//flushing outputs
output reg      flushD
);

always@(*)
begin
    if( (rs1E == rdM) && regwrM && rs1E != 0 )
        begin
            forwardAE = 2'b10 ;
        end
    else if( (rs1E == rdW) && regwrW && rs1E != 0 )
        begin
            forwardAE = 2'b01 ;
        end
    else
        begin
            forwardAE <= 2'b00 ;
        end

    if( (rs2E == rdM) && regwrM && rs2E != 0 )
        begin
            forwardBE = 2'b10 ;
        end
    else if( (rs2E == rdW) && regwrW && rs2E != 0 )
        begin
            forwardBE = 2'b01 ;
        end
    else
        begin
            forwardBE = 2'b00 ;
        end

end

always@(*)
begin
    if(rst)
        begin
            stallF = 1'b0 ;
            stallD = 1'b0 ;
        end
    else if(( (rdE == rs1D) || (rdE == rs2D) ) && resultsrcE0 )
        begin
            stallF = 1'b1 ;
            stallD = 1'b1 ;
        end
    else
        begin
            stallF = 1'b0 ;
            stallD = 1'b0 ;
        end
end

always@(*)
begin
    if(rst)
        begin
            flushD = 1'b0 ;
        end
    else if(PCsrcE0)
        begin
            flushD = 1'b1 ;
        end
    else
        begin
            flushD = 1'b0 ;
        end
end

```

```

if(rst)
begin
flushE = 1'b0 ;
end
else if((( rdE == rs1D) || (rdE == rs2D) ) && resultsrcE0 ) || PCsrcE0)
begin
flushE = 1'b1 ;
end
else
begin
flushE = 1'b0 ;
end
end

endmodule

```

3.15 top_RISCV

```

module top_RISCV #(parameter n = 10 , m = 32)(
input wire clk,
input wire rst,
input wire [31:0] instrF,
output wire [n-1:0] addr,
output wire [m-1:0] write_dataM,
output wire memwrM,
output wire [31:0] read_dataM,
output wire [31:0] PCF,
output wire [31:0] instrD
);

wire [1:0] PCsrc ;
wire [1:0] immsrcD ;
wire ALUsrcD ;
wire [1:0] ALUctrlD ;
wire [1:0] resultsrcD ;
wire regwrD , regwrM , regwrW ;
wire [31:0] ALUoutM ;
wire [1:0] forwardAE, forwardBE;
wire [4:0] rs1E , rs2E ;
wire [4:0] rdE ,rdM , rdW ;
wire [4:0] rs1D , rs2D ;
wire jumpD ,jalrD , branchD ;
wire stallF , stallD, flushD , flushE ;
wire resultsrcE0 , PCsrcE0 ;

assign addr = ALUoutM[9:0] ;

datapath u_dp (
.clk(clk),
.rst(rst),
//instr memory inputs
.instrF(instrF),
//data memory inputs
.read_dataM(read_dataM),
//CU inputs
.immsrcD(immsrcD),
.ALUsrcD(ALUsrcD),
.ALUctrlD(ALUctrlD),
.resultsrcD(resultsrcD),
.regwrD(regwrD),
.jumpD(jumpD),
.jalrD(jalrD),
.branchD(branchD),
.memwrD(memwrD),
//hazard unit inputs
.forwardAE(forwardAE),
.forwardBE(forwardBE),
.stallF(stallF),
.stallD(stallD),
.flushE(flushE),
.flushD(flushD),
//CU outputs
.instrD(instrD),

```

```

//hazard unit outputs
.rs1E(rs1E),
.rs2E(rs2E),
.rdM(rdM),
.rdW(rdW),
.regwrM(regwrM),
.regwrW(regwrW),
.rs1D(rs1D),
.rs2D(rs2D),
.rdE(rdE),
.resultsrcE0(resultsrcE0),
.PCsrcE0(PCsrcE0),
//instr memory outputs
.PCF(PCF),
//data memory outputs
.ALUoutM(ALUoutM),
.write_dataM(write_dataM),
.memwrM(memwrM)
);

control_unit u_cu (
.opD(instrD[6:0]),
.funct3D(instrD[14:12]),
.funct7_5D(instrD[30]),
//datapath outputs
.immsrcD(immsrcD),
.ALUsrcD(ALUsrcD),
.ALUctrlD(ALUctrlD),
.resultsrcD(resultsrcD),
.regwrD(regwrD),
.jumpD(jumpD),
.jalrD(jalrD),
.branchD(branchD),
//data memory output
.memwrD(memwrD)
);

hazard_unit u_hu (
.rst(rst),
.rs1E(rs1E),
.rs2E(rs2E),
.rdM(rdM),
.rdW(rdW),
.regwrM(regwrM),
.regwrW(regwrW),
//stalling inputs
.rs1D(rs1D),
.rs2D(rs2D),
.rdE(rdE),
.resultsrcE0(resultsrcE0),
//flushing inputs
.PCsrcE0(PCsrcE0),
//forwarding outputs
.forwardAE(forwardAE),
.forwardBE(forwardBE),
//stalling outputs
.stallF(stallF),
.stallD(stallD),
.flushE(flushE),
//flushing outputs
.flushD(flushD)
);

endmodule

```

3.16 instr_rom

```
module instr_rom #(parameter n = 10 , m = 32 ) (
input wire [n-1:0] addr,
output wire [m-1:0] read_data
);

reg [m-1:0] mem [0:2**(n-2)-1] ; //n-2 for word addressable memory

initial
begin
    $readmemh("testcases.txt", mem);
end

assign read_data = mem[addr[n-1:2]] ; //[n-1:2] for word addressable memory

endmodule
```

3.17 data_ram

```
module data_ram #(parameter n = 10 , m = 32 ) (
input wire clk,
input wire rst,
input wire we,
input wire [n-1:0] addr,
input wire [m-1:0] write_data,
output wire [m-1:0] read_data
);

reg [m-1:0] mem [0:2**(n-1)-1] ;
integer i ;

always@(posedge clk or posedge rst)
begin
    if(rst)
        begin
            for(i=0 ; i < 2**(n-1) ; i = i+1)
                begin
                    mem[i] <= 'h0 ;
                end
            end
        else if(we)
            begin
                mem[addr[n-1:2]] <= write_data ;
            end
        end

    assign read_data = mem[addr[n-1:2]] ;

endmodule
```

4.simulation

4.1 top_RISCV_tb

```
`timescale 1ps/1fs
module top_RISCV_tb #(parameter n = 10 , m = 32) ();
reg clk ;
reg rst ;
wire [31:0] instrF ;
wire [n-1:0] addr;
wire [m-1:0] write_dataM;
wire      memwrM ;
wire [31:0] read_dataM;
wire [31:0] PCF;
wire [31:0] instrD;

//instantiation
top_RISCV #(10,32) u_top (
.clk(clk),
.rst(rst),
.instrF(instrF),
.addr(addr),
.write_dataM(write_dataM),
.memwrM(memwrM),
.read_dataM(read_dataM),
.PCF(PCF),
.instrD(instrD)
);

instr_rom #(10,32) u_ins_rom (
.addr(PCF[9:0]),
.read_data(instrF)
);

data_ram #(10,32) u_data_ram (
.clk(clk),
.rst(rst),
.we(memwrM),
.addr(addr),
.write_data(write_dataM),
.read_data(read_dataM)
);

initial
begin
    clk = 0 ;
    forever #250 clk = ~clk ; //clk with period 500ps
end

initial
begin
    rst = 1'b1 ;
    #500
    rst = 1'b0 ;
end
```

```

always@(negedge clk)
begin
    if(memwrM)
        begin
            if(write_dataM == 2 && addr == 96)
                begin
                    $display("time = %0t , write_dataM = %4d , addr = %8d ,testcase1 passed (first sw)",
$time , write_dataM , addr) ;
                    end
                else if(write_dataM == 4 && addr == 92)
                    begin
                        $display("time = %0t , write_dataM = %4d , addr = %8d ,testcase2 passed (second
sw)", $time , write_dataM , addr) ;
                        #500
                        $stop ;
                    end
                else
                    begin
                        $display("time = %0t , write_dataM = %4d , addr = %8d ,testcase1,2 failed", $time ,
write_dataM , addr) ;
                        $stop ;
                    end
            end
        end
    end
endmodule

```

4.2 assembly code and its output

| | |
|------------------------|---|
| main: addi x2, x0, 5 | # x2 = 5 0 00500113 |
| addi x3, x0, 12 | # x3 = 12 4 00C00193 |
| addi x7, x3, -9 | # x7 = (12 - 9) = 3 8 FF718393 |
| or x4, x7, x2 | # x4 = (3 OR 5) = 7 C 0023E233 |
| and x5, x3, x4 | # x5 = (12 AND 7) = 4 10 0041F2B3 |
| add x5, x5, x4 | # x5 = 4 + 7 = 11 14 004282B3 |
| beq x5, x7, end | # shouldn't be taken 18 02728463 |
| beq x4, x0, around | # shouldn't be taken 1C 00020463 |
| addi x5, x0, 0 | # x5 = 0 + 0 = 0 20 00000293 |
| around: add x7, x4, x5 | # x7 = (7 + 0) = 7 24 005203B3 |
| sub x7, x7, x2 | # x7 = (7 - 5) = 2 28 402383B3 |
| sw x7, 84(x3) | # [96] = 2 2C 0471AA23 (testcase1) |
| lw x2, 96(x0) | # x2 = [96] = 2 30 06002103 |


add x9, x2, x5 # $x9 = (2 + 0) = 2$ 34 005104B3
 jal x3, end # jump to end, x3 = 0x3C 38 008001EF
 addi x2, x0, 1 # shouldn't execute 3C 00100113
 end: add x2, x2, x9 # $x2 = (2 + 2) = 4$ 40
 sw x2, 0x20(x3) # **[92]** = **4** 44 0221A023 (testcase2)
 done: beq x2, x2, done # infinite loop 48 00210063

testcases.txt content

```

00500113
00C00193
FF718393
0023E233
0041F2B3
004282B3
02728463
00020463
00000293
005203B3
402383B3
0471AA23
06002103
005104B3
008001EF
00100113
00910133
0221A023
00210063
  
```


4.3 simulation results

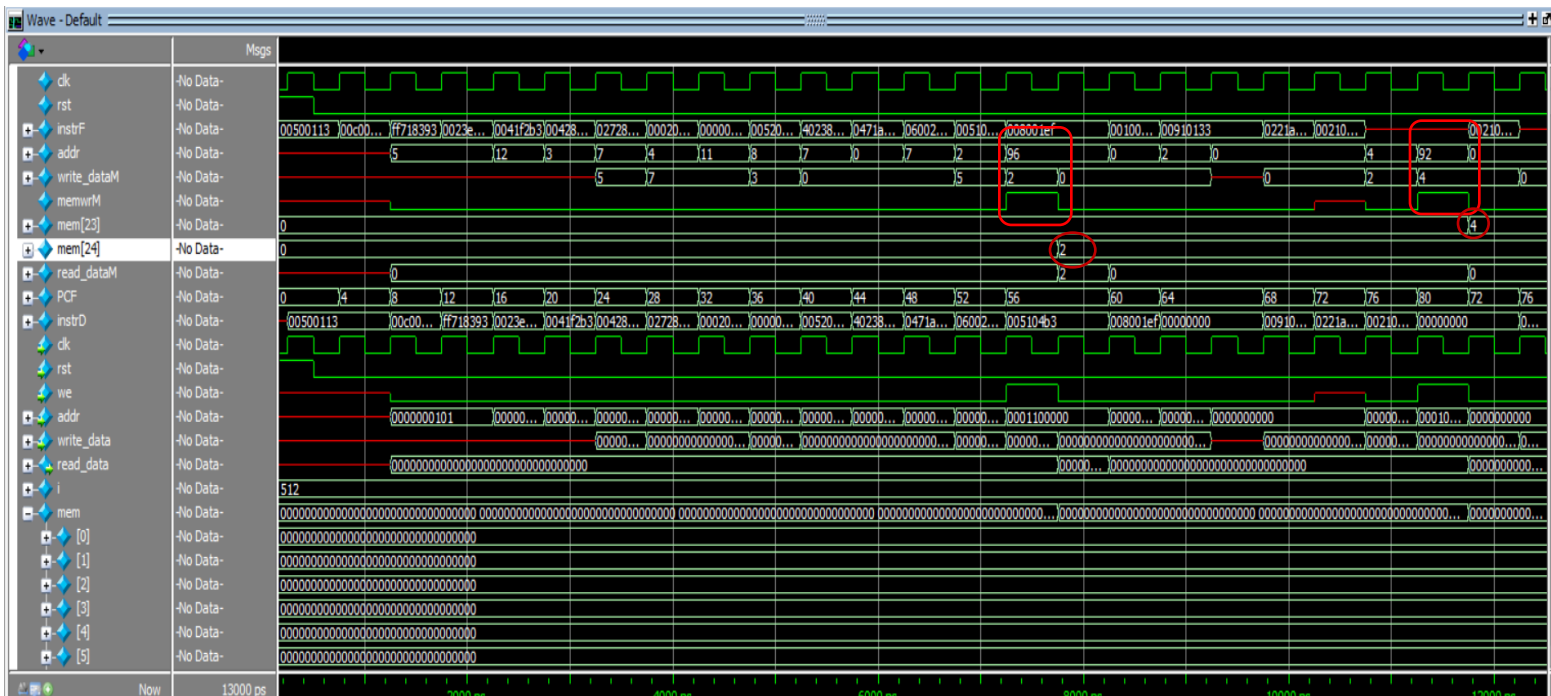

$\text{mem}[23]_{\text{word addressable}} = \text{mem}[23 \times 4] = \text{mem}[92] = 4$

$\text{mem}[24]_{\text{word addressable}} = \text{mem}[24 \times 4] = \text{mem}[96] = 2$

```
VSIM 12> run -all
# time = 7500000 , write_dataM = 2 , addr = 96 ,testcase1 passed (first sw)
# time = 11500000 , write_dataM = 4 , addr = 92 ,testcase2 passed (second sw)
```